

EXPERIMENT-1

Realization of Adder & Subtractor

Aim: To realise full adder / subtractor using
(i) Basic gates (ii) Universal gates

SOFTWARE: CircuitVerse / Multiverse, Multisim 14, IC740
IC Trainer kit, IC7401, IC7432, IC7400, IC7404

THEORY

Full Adder Theory

Full Adder: It takes 3 inputs & produces 2 outputs
first two inputs are A & B and third one
is Carry-in

The outputs are Cout & S [Sum]

A full adder is designed in such a manner that it can take
& inputs and creates a byte wide adder and
cascade the carry bit from one adder to another.




Full subtractor

A full subtractor is a conventional circuit that performs
subtractions of two bits, one is minuend and other
is subtrahend, taking into account borrow of previous
adjacent lower minuend. The circuit has 3 input
& 2 output.

ADDERS

-K-map, Circuit Diagrams, truth table (Simulations)

(1) Half Adder

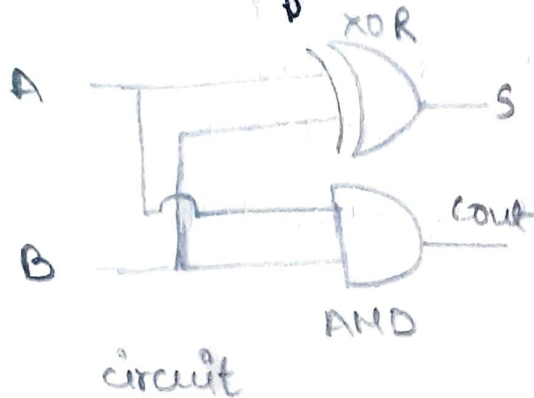

INPUT		OUTPUT	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	0	1
1	1	0	1

$$A \oplus B$$

B	0	1
A	0	1
0	0	1
1	1	0

$$A \cdot B$$

B	0	1
A	0	1
0	0	0
1	0	1

Half Adder = $A \oplus B$ for

$A \cdot B$ for carry of p


(2) Full Adder

Input			Output	
A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


BC	00	01	11	10
A	0	0	1	0
0	0	1	0	1
1	1	0	1	0

B	00	01	11	10
A	0	0	1	0
0	0	1	0	1
1	1	0	1	0


FULL ADDER USING LOGIC GATES

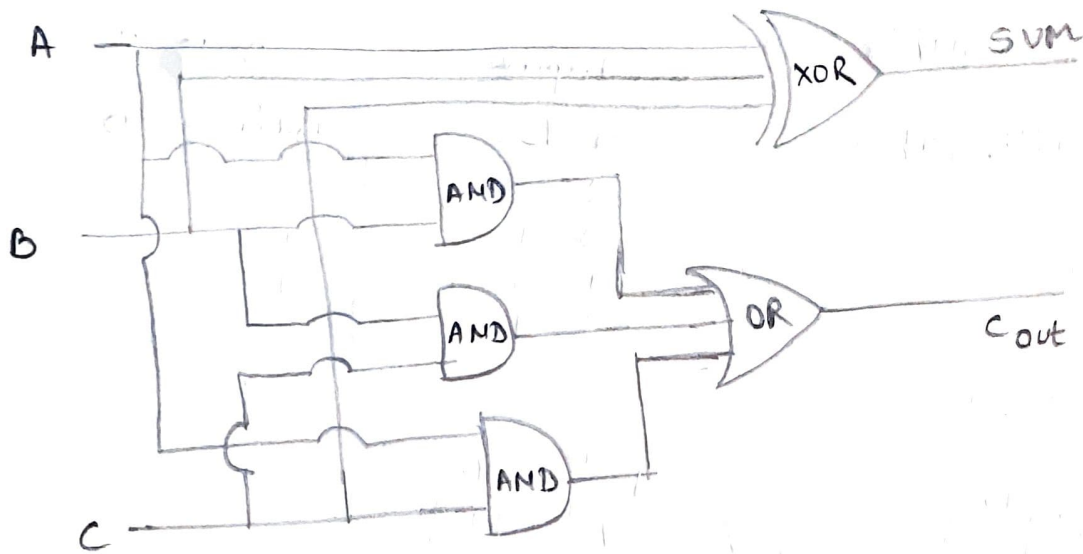

FULL ADDER USING NAND

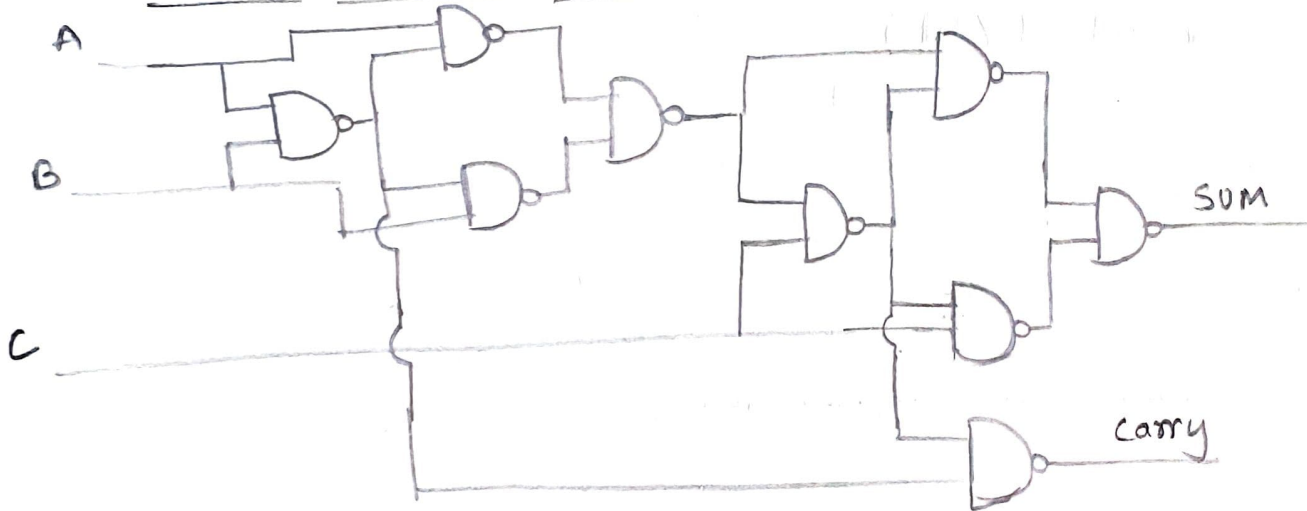

FULL ADDER USING NOR

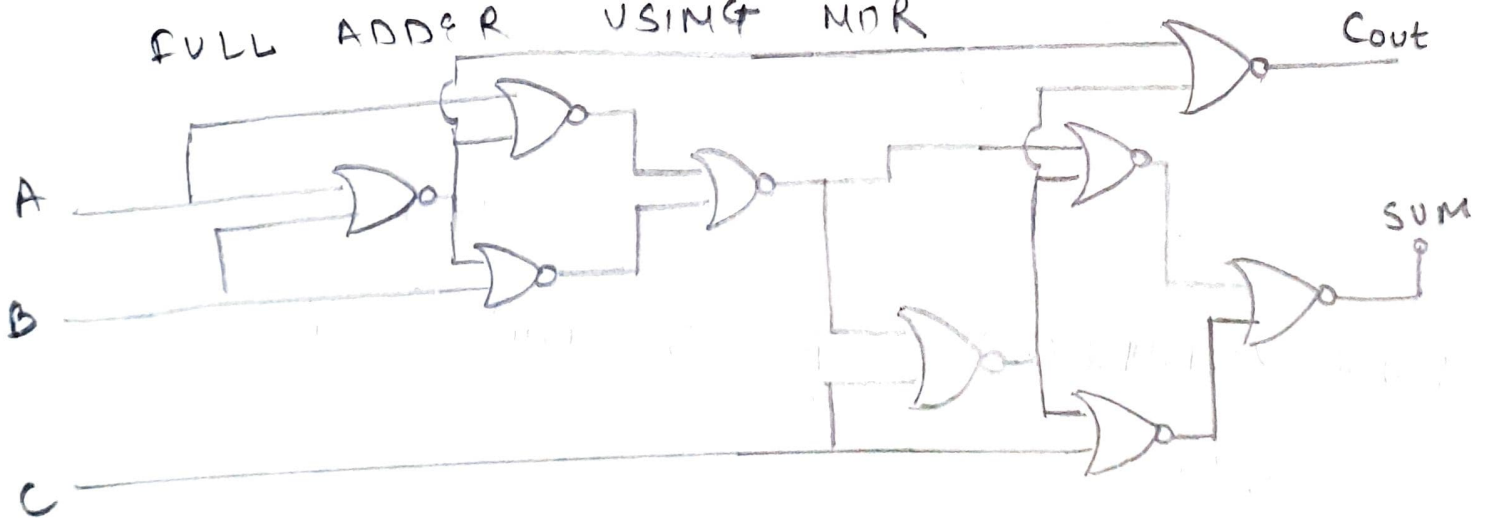

SUBTRACTOR

Truth table, karnaugh-map circuit, simulator

(1) Half-Subtractor

Truth Table


Input		Output	
A	B	Diff	Bor
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Difference


A	B	\bar{A}	\bar{B}
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0	0

A	B	\bar{A}	\bar{B}
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0	0

$A \oplus B$ (XOR)

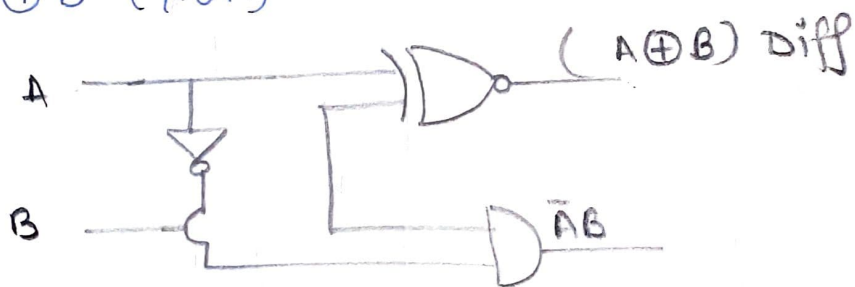

Subtractor using Basic gate

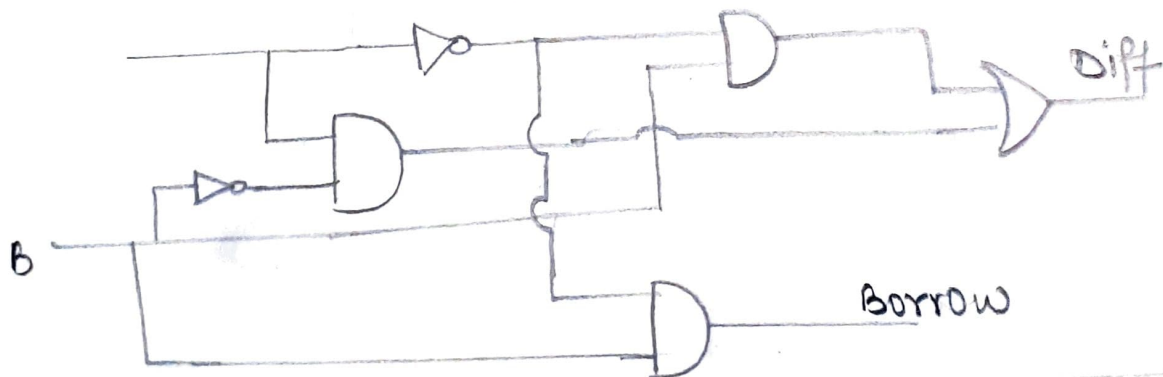

FULL SUBTRACTOR

truth table

A	B	B _{in}	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


k-map

A \ BC				
	00	01	11	10
0	0	1	0	1
1	1	0	1	0


A \ BC				
	00	01	11	10
0	0	1	1	1
1	0	0	1	0

Diff - $A \oplus B \oplus C$


Bor - $A'C + A'B + BC$

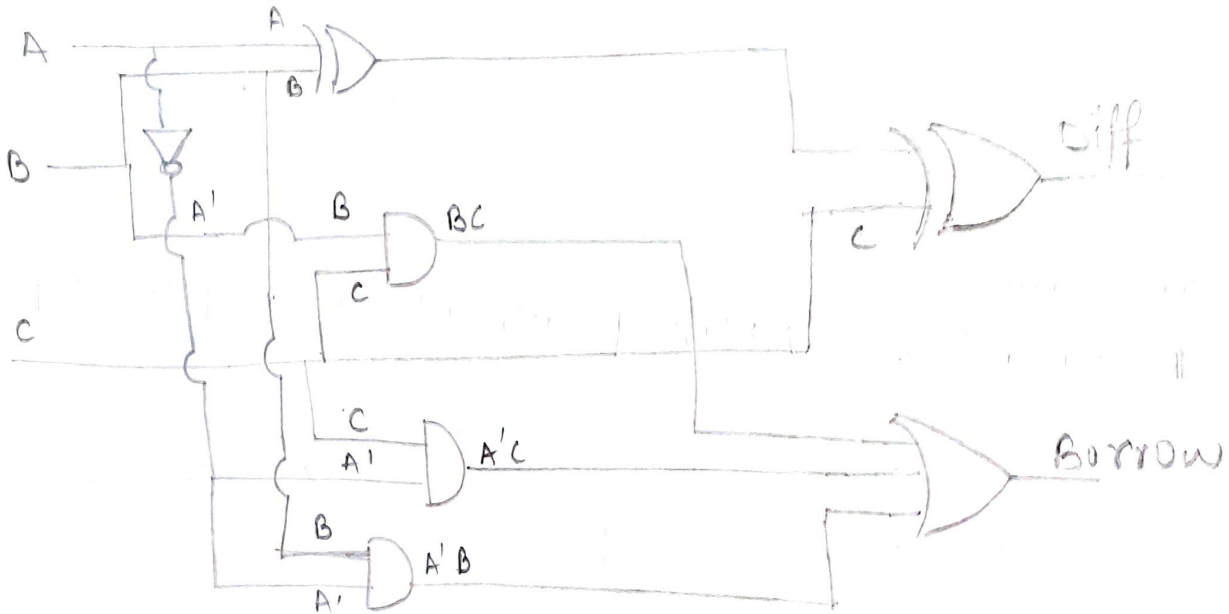

FULL SUBTRACTOR USING NAND

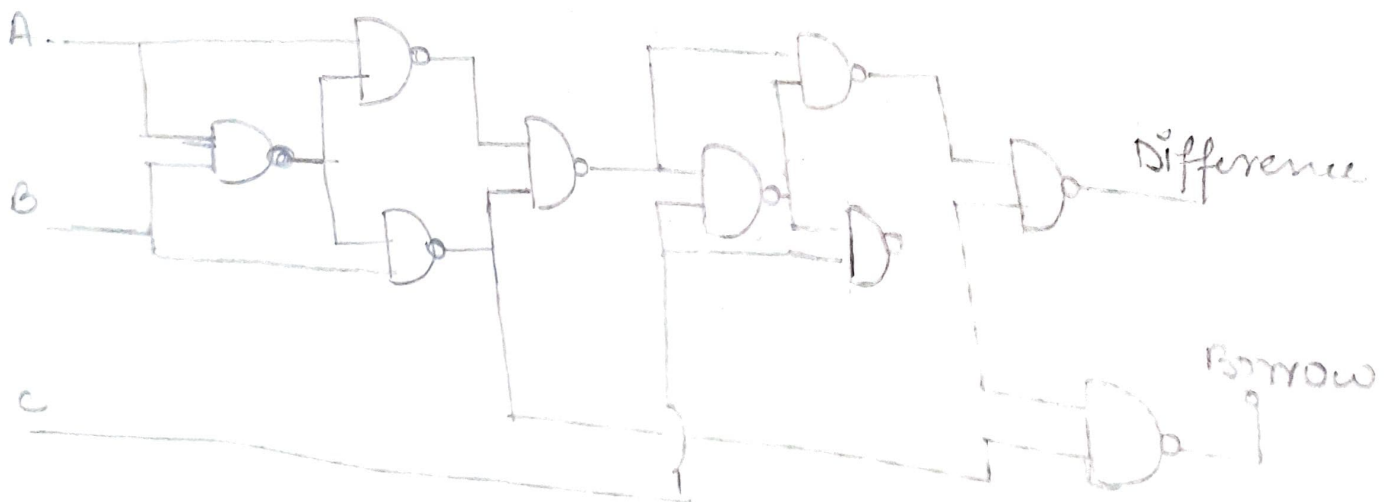

FULL SUBTRACTOR USING NOR

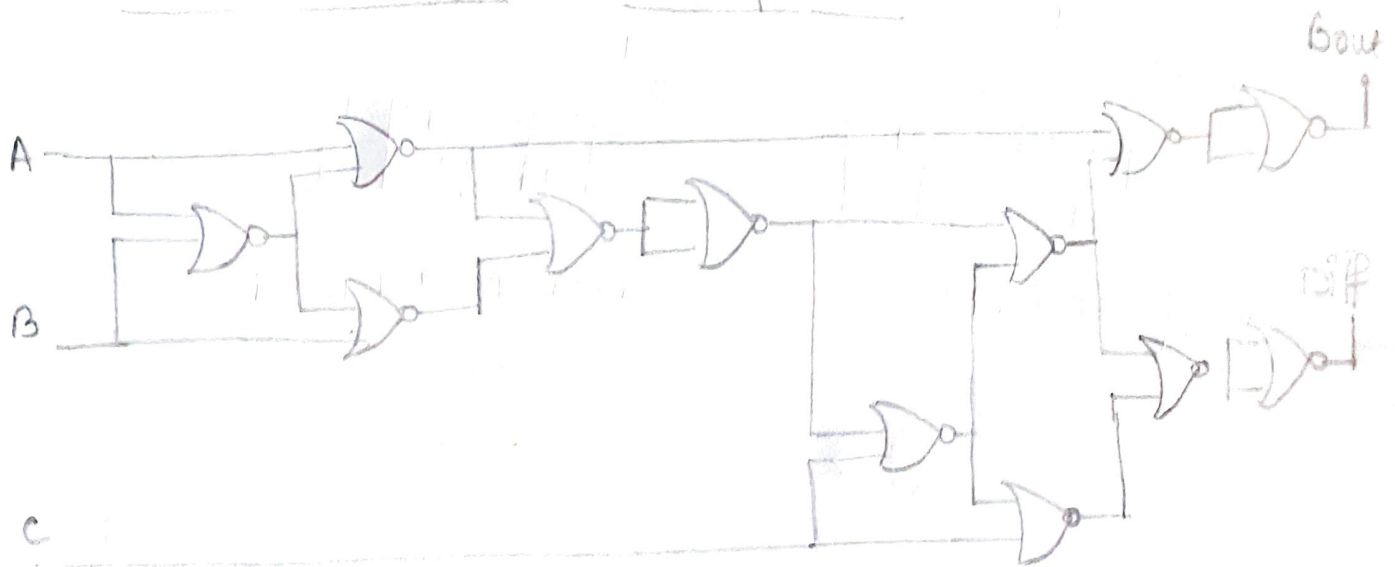

Conclusion:

Realization of Adder & Subtractor successfully implemented